

Question 2:

⊗ 1-bit subtractor


- Half subtractor

X	Y	D	b _{out}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

b_{out} = 1
 $\begin{array}{r} 0 \quad 1 \\ - 1 \quad 0 \\ \hline 0 \quad 1 \end{array}$
 different

⇒ Expression: $D = X \oplus Y$
 $b_{out} = \bar{X}Y$

Circuit:

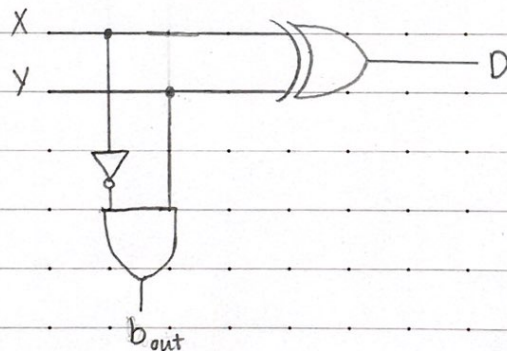

- Full subtractor :

X	Y	b _{in}	D	b _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

→ 0-1 = 1 (above), borrow 1; 1-0 = 1

→ 0-1 = 1 (above), borrow 1; 1-1 = 0


(X - Y - b_{in})

⇒ Expression:


$$\begin{aligned}
 D &= X'Y'b_{in} + X'Yb'_{in} + XY'b_{in} + XYb_{in} \\
 &= b'_{in}(X'Y + XY') + b_{in}(X'Y' + XY) \\
 &= b'_{in}(\underbrace{X \oplus Y}_A) + b_{in}(\underbrace{X \odot Y}_{A'}) \\
 &= b_{in} \oplus (X \oplus Y)
 \end{aligned}$$

$$\begin{aligned}
 b_{out} &= X'Y'b_{in} + X'Yb'_{in} + X'Yb_{in} + XYb_{in} \\
 &= X'Y(b'_{in} + b_{in}) + b_{in}(X'Y' + XY) \\
 &= X'Y + b_{in}(X \odot Y) \\
 &= X'Y + b_{in}(X \oplus Y)'
 \end{aligned}$$

Circuit

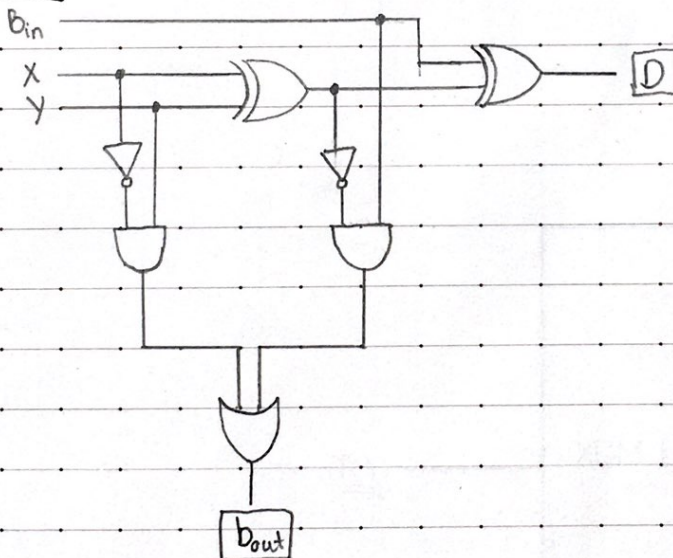


⊗ 4 bit subtractor.

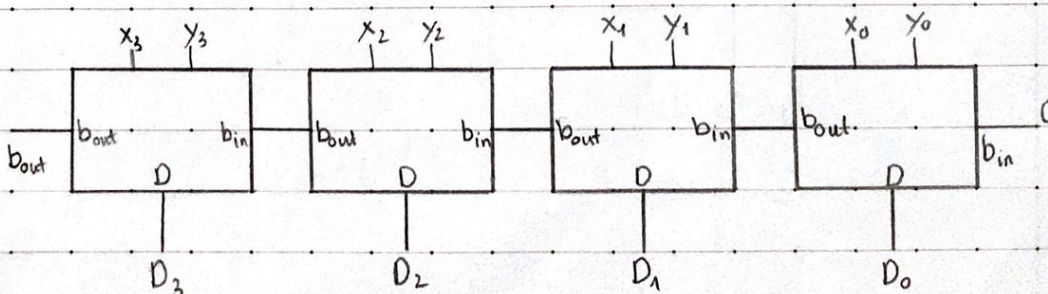

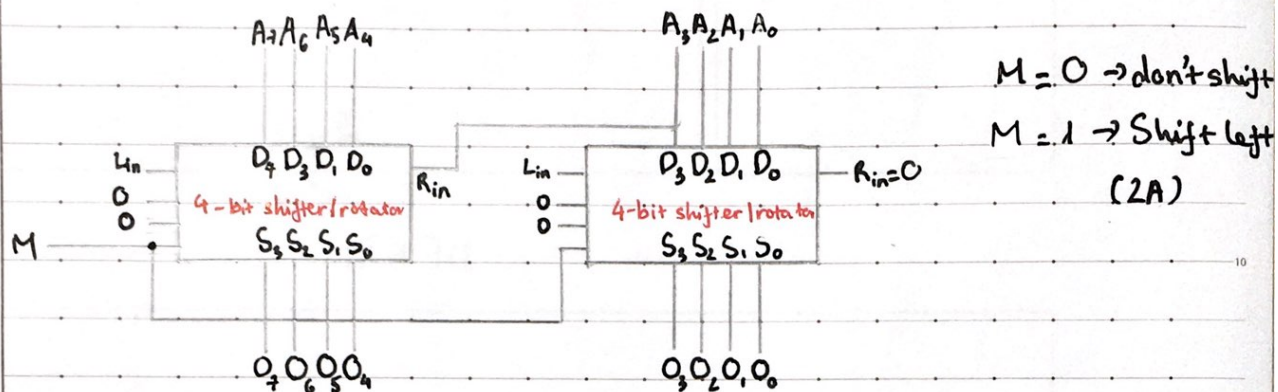
Question 5:

⊗ 8-bit shifter from 4-bit shifter

- Note: only keep left shifter and non-shift back (since we don't need other function)



⊗ 8-bit binary full adder.

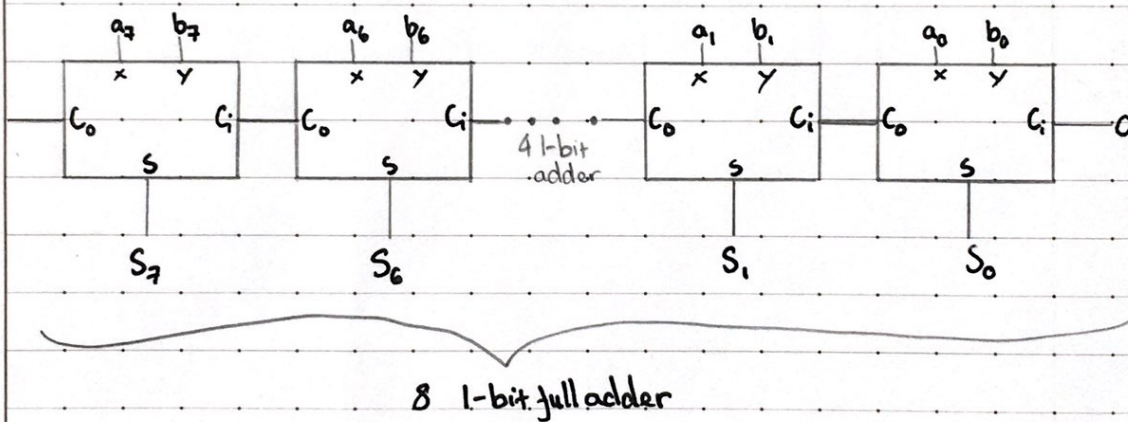

⊗ The circuit:


- Note

+ The table shows that:

- Value of A depends on control input M_1 ($A \approx M=0$, $2A \approx M=1$)
- Value of B depends on control input M_2 ($2B \approx M=0$, $4B \approx M=1$)
- + Since value of B is not needed, but only $2B$ and $4B$

→ Always shift B one time, then let it go through a shifter control by M_0 , where it either shifts again ($4B$) or don't shift ($2B$)

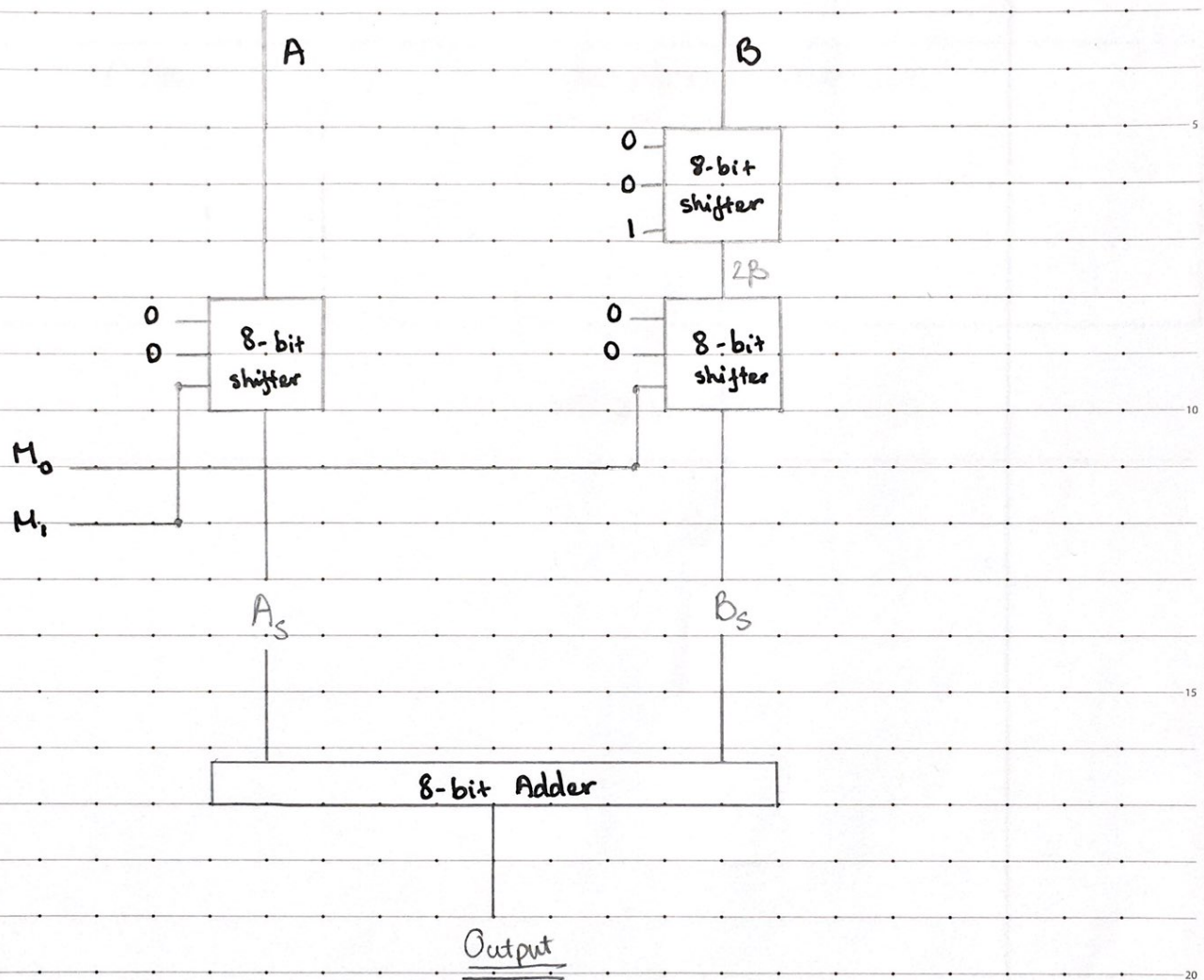+ 8 bit shifter & 8 bit adder has been drawn in detailed above. Below these two components are drawn in blocks.



+ $M_1 = 0 \rightarrow A$ don't shift $\rightarrow A$
 $= 1 \rightarrow A$ shift left $\rightarrow 2A$
 + $M_0 = 0 \rightarrow 2B$ don't shift $\rightarrow 2B$
 $= 1 \rightarrow 2B$ shift left $\rightarrow 4B$