

You need to make your answers more clear. Label the specific part of the question you are answering and make direct answers stand out from explanations

14/21

 


Figure 3-15. A 1-bit left/right shifter.

From  $S_1 \rightarrow S_6$ : since the number of gates involve to produce the output is the same

$\rightarrow$  delay =  $S_1 = 16\text{ns}$  (1 inverter, 2 and gates, 1 or gate)

For  $S_0$ : delay =  $4 + 4 = 8\text{ns}$  (1 inverter, 1 and gate)

For  $S_7$ : delay =  $4\text{ns}$  (1 and gate)

-2  
 $\rightarrow$  Stable output after: 16 ns X  
 3 gates,  $3 \times 4\text{ns} = 12\text{ns}$

Which is your answer? Find the longest path and do the calculation for that path since we want the max time

- 2

6 gates,  $6 \times 4 \text{ ns} = 24 \text{ ns}$

→ For AB case

+ Time to get to the red circle

$$4 + 4 + 4 + 4 = 16 \text{ ns}$$

+ Time to wait for decoder

$$4 + 4 + 4 = 12 \text{ ns}$$

→ Time to get to the purple circle

$$16 + 12 = 28 \text{ ns}$$

Assume that results of 4 lines of decoders are simultaneous → like if line 1 = 1 then we know other lines = 0 (and that if the AND gate have 1 input = 0 then the output = 0)

→ Stable output after:  $28 + 4 = 32 \text{ ns}$


→ For A+B and  $\bar{B}$  case

+ Time to get to red circle = 16 ns (see above)

+ Time to wait for decoder

$$4 + 4 = 8 \text{ (ns)}$$

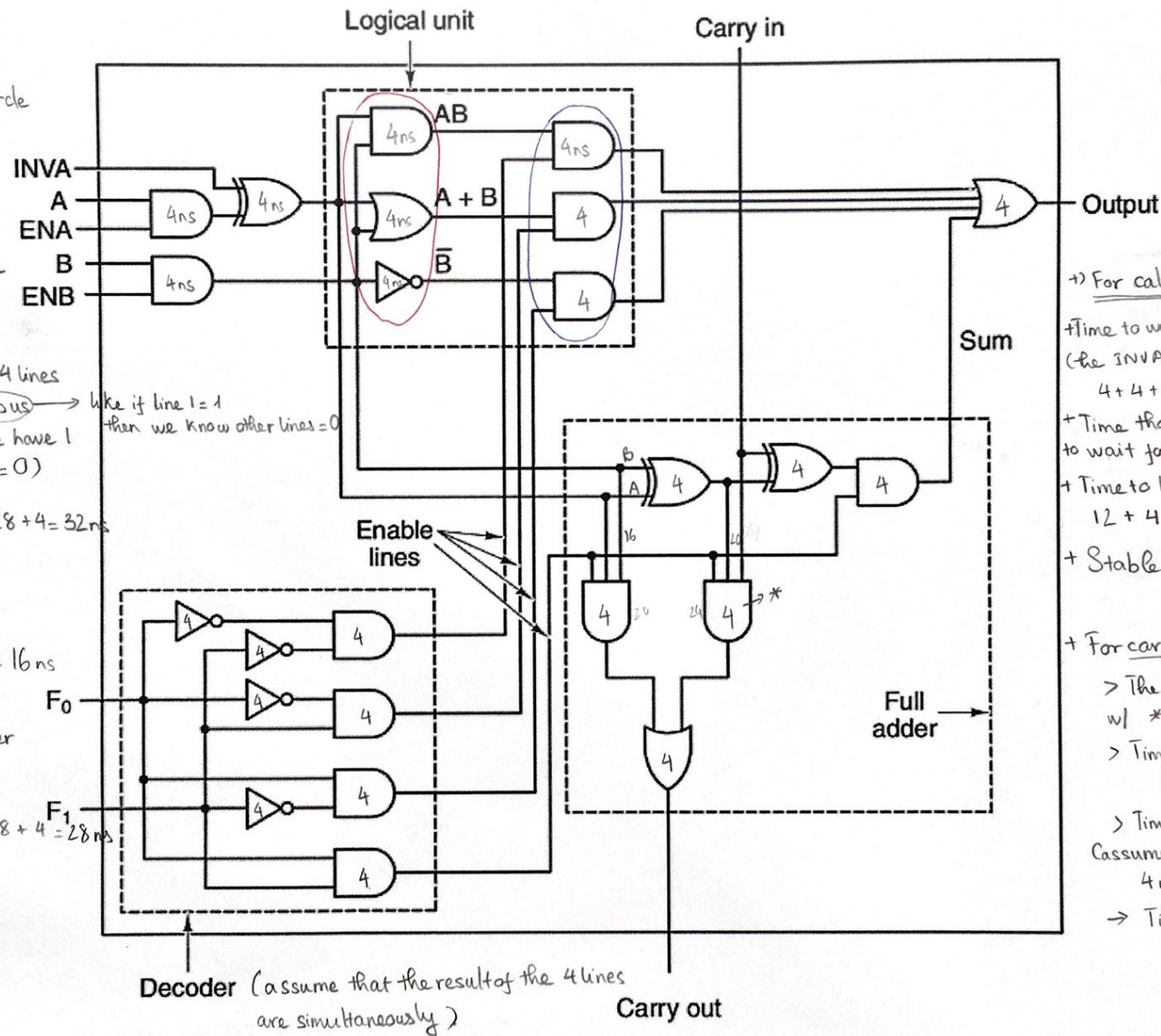→ Stable output after:  $16 + 8 + 4 = 28 \text{ ns}$



→ For calculating sum

+ Time to wait for A & B input (the INVA, ENBA, ENB part)

$$4 + 4 + 4 = 12 \text{ ns}$$

+ Time that the final AND gate have to wait for decoder: 4 ns

+ Time to have the sum:

$$12 + 4 + 4 + 4 + 4 = 28 \text{ ns}$$

+ Stable output after:  $28 + 4 = 32 \text{ ns}$

+ For carry out

> The AND gate that marked w/ \* takes longer wait time

> Time to wait for XOR output:  $12 + 4 = 16 \text{ ns}$

> Time to wait for decoder Assume that it doesn't run in parallel 4 ns


→ Time till stable carry out:

$$16 + 4 + 4 + 4 = 28 \text{ ns}$$

↓   ↓  
AND OR

Figure 3-18. A 1-bit ALU.



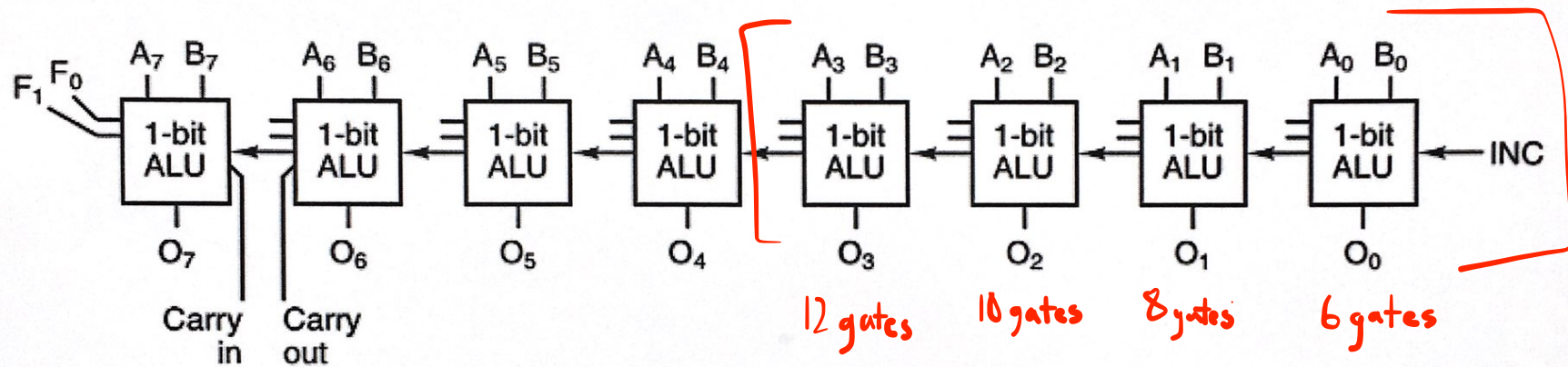

**Figure 3-19.** Eight 1-bit ALU slices connected to make an 8-bit ALU. The enables and invert signals are not shown for simplicity.

+ For logic calculation  $(AB, A+B, \bar{B})$ : stable output after  $pd \times 8 = \begin{cases} 32 \times 8 = 256 \text{ ns} \\ 28 \times 8 = 224 \text{ ns} \end{cases}$

+ For arithmetic addition: for the 1st  $A_0B_0$  bit: 32 ns

for bit from  $A_1B_1 \rightarrow A_7B_7$ :  $32 + 28 = 60 \text{ ns}$

way for carry in (assume calculation of carry in and sum are not parallel)

$\rightarrow$  Stable output after:  $60 \times 7 + 32 = 452 \text{ ns}$  ✗

max length path = 12 gates  
 $12 \times 4 \text{ ns} = 48 \text{ ns}$

-3