

Question 2: 17/20

⊗ 1-bit subtractor


- Half subtractor

X	Y	D	b _{out}
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

b_{out} = 1
 $\begin{array}{r} 0 \quad 1 \\ - 1 \quad 0 \\ \hline 0 \quad 1 \end{array}$
 different

⇒ Expression: $D = X \oplus Y$
 $b_{out} = \bar{X}Y$

Circuit:

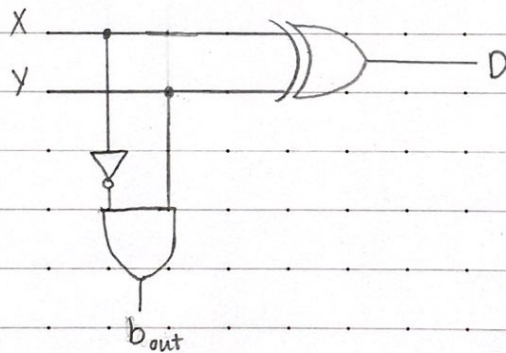

- Full subtractor :

X	Y	b _{in}	D	b _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



→ 0-1 = 1 (above), borrow 1; 1-0 = 1

→ 0-1 = 1 (above), borrow 1; 1-1 = 0

(X - Y - b_{in})

⇒ Expression:

$$D = X'Y'b_{in} + X'Yb'_{in} + XY'b_{in} + XYb_{in}$$

$$= b'_{in}(X'Y + XY') + b_{in}(X'Y' + XY)$$

$$= b'_{in}(\underbrace{X \oplus Y}_A) + b_{in}(\underbrace{X \odot Y}_{A'})$$

- | show the laws/rules you used

$$= b_{in} \oplus (X \oplus Y) \checkmark$$

$$b_{out} = X'Y'b_{in} + X'Yb'_{in} + X'Yb_{in} + XYb_{in}$$


$$= X'Y(b'_{in} + b_{in}) + b_{in}(X'Y' + XY)$$

$$= X'Y + b_{in}(X \odot Y)$$


- | show the laws/rules you used

$$= X'Y + b_{in}(X \oplus Y)' \checkmark$$

Circuit

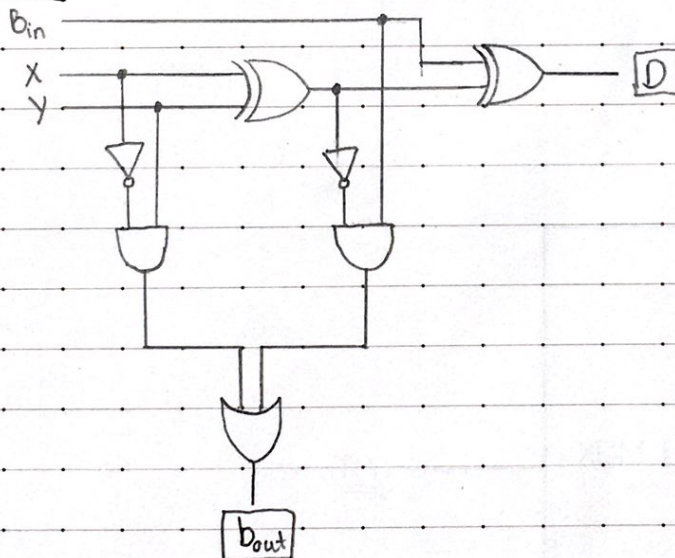


⊗ 4 bit subtractor.

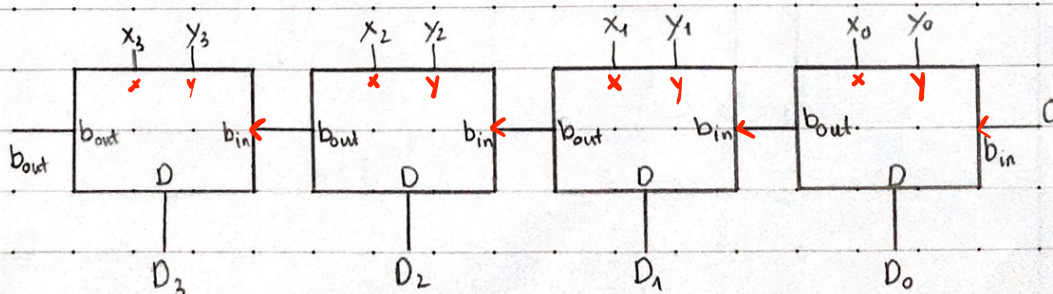

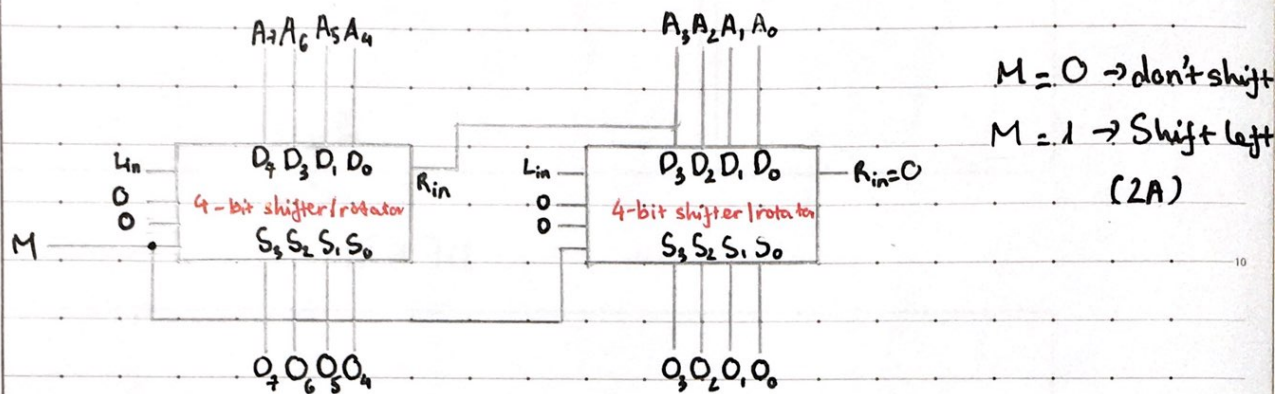
Question 5: 19/22

* 8-bit shifter from 4-bit shifter

- Note: only keep left shifter and non-shift back (since we don't need other function)



* 8-bit binary full adder.

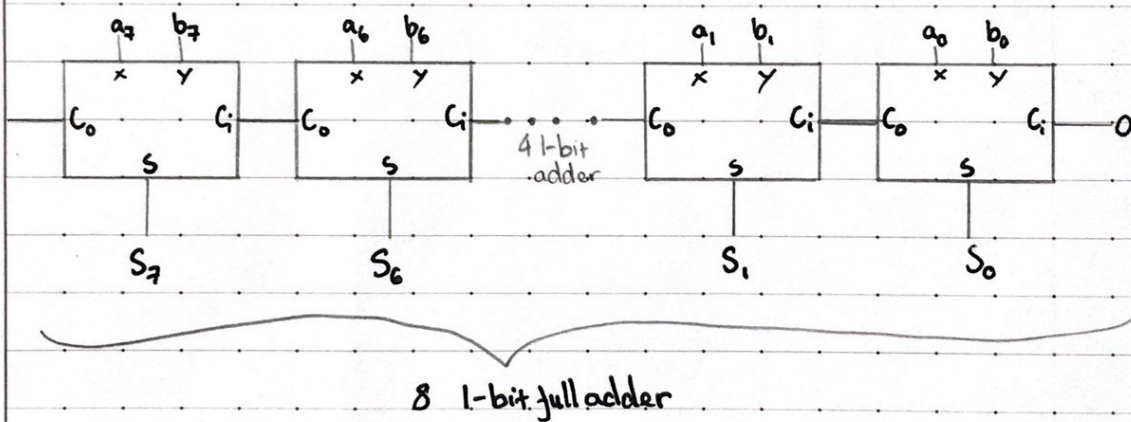

* The circuit:

- Note


+ The table shows that:

- Value of A depends on control input M_1 ($A \approx M=0$, $2A \approx M=1$)
- Value of B depends on control input M_2 ($2B \approx M=0$, $4B \approx M=1$)

+ Since value of B is not needed, but only 2B and 4B

→ Always shift B one time, then let it go through a shifter control by M_0 , where it either shifts again (4B) or don't shift (2B)

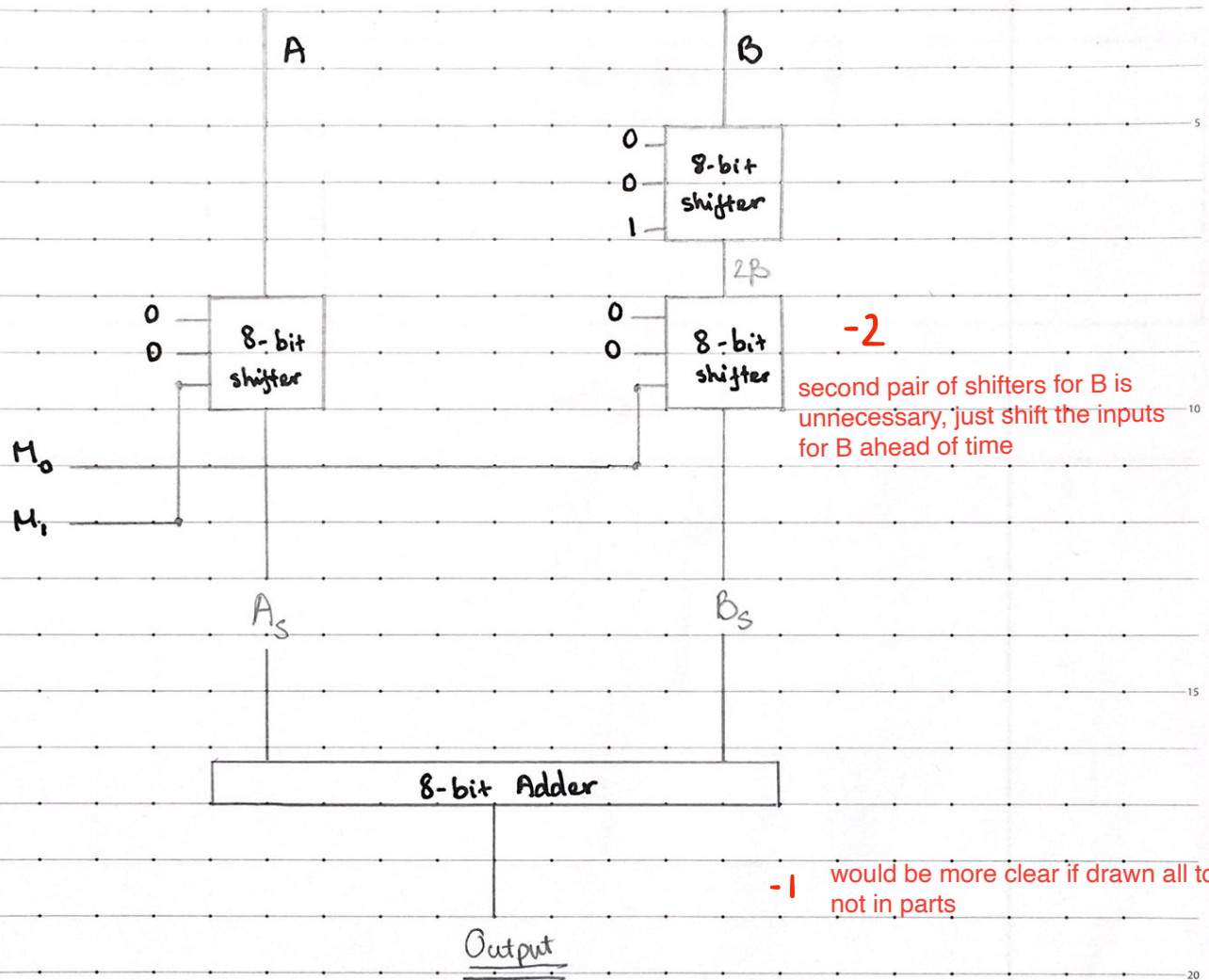+ 8 bit shifter & 8 bit adder has been drawn in detailed above. Below these two components are drawn in blocks.



+ $M_1 = 0 \rightarrow A$ don't shift $\rightarrow A$
 $= 1 \rightarrow A$ shift left $\rightarrow 2A$
 + $M_0 = 0 \rightarrow 2B$ don't shift $\rightarrow 2B$
 $= 1 \rightarrow 2B$ shift left $\rightarrow 4B$